
1. Selesai kan table kebenaran berikut.

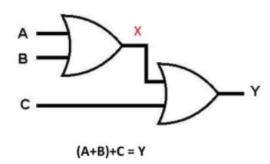Soal Latihan2

Tentukan tabel kebenaran dari rangkaian gerbang OR dibawah ini.



Α	В	X	С	Υ
0	0		0	
0	0		1	
0	1		0	
0	1		1	
1	0		0	
1	0		1	
1	1		0	
1	1		1	

KUMPULKAN DENGAN FORMAT .PDF PERT3_NAMA_NPM_KELAS.pdf

Α	В	С	Υ
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1